

CSE 305 (Computer Architecture)

January 2021

Class Test 1

Full Time: 25 minutes (including upload time)

Full Marks: 20

Instructions

- In this class test, you have to
 - Write down the answers in a paper,
 - Scan the paper using mobile camera/any other scanner,
 - Convert the scanned image to a pdf,
 - Rename the pdf with your student id, and
 - Finally, upload the pdf to the Moodle.
- Write down your student id and name first.
- It is a closed book exam. DO NOT copy from any other person or source. Be fair. Be honest.
- See the format in the following page.

Questions:

1.	<p>A program contains 3 multiplication instructions and 2 addition instructions. Based on this program, compare the performance of computer A and computer B where</p> <p>a. In computer A, each multiplication instruction requires 3 clock cycles and each addition instruction requires 2 clock cycles. The cycle time of computer A is 500ps.</p> <p>b. In computer B, each multiplication instruction requires 4 clock cycles and each addition instruction requires 1 clock cycle. The cycle time of computer B is 450ps.</p>	(8)																												
2.	<p>Derive the input equations (X_i, Y_i and Z_i) for the parallel adders to be used in the ALU which satisfies the following functional design specification.</p> <table><tr><th>S_2</th><th>S_1</th><th>C_{in}</th><th>Required Functions</th></tr><tr><td>0</td><td>0</td><td>0</td><td>$F = AB + C$</td></tr><tr><td>0</td><td>0</td><td>1</td><td>$F = AB + C + 1$</td></tr><tr><td>0</td><td>1</td><td>0</td><td>$F = AB$</td></tr><tr><td>0</td><td>1</td><td>1</td><td>$F = AB + 1$</td></tr><tr><td>1</td><td>0</td><td>x</td><td>$F = (AB)'$</td></tr><tr><td>1</td><td>1</td><td>x</td><td>$F = AB$</td></tr></table>	S_2	S_1	C_{in}	Required Functions	0	0	0	$F = AB + C$	0	0	1	$F = AB + C + 1$	0	1	0	$F = AB$	0	1	1	$F = AB + 1$	1	0	x	$F = (AB)'$	1	1	x	$F = AB$	(12)
S_2	S_1	C_{in}	Required Functions																											
0	0	0	$F = AB + C$																											
0	0	1	$F = AB + C + 1$																											
0	1	0	$F = AB$																											
0	1	1	$F = AB + 1$																											
1	0	x	$F = (AB)'$																											
1	1	x	$F = AB$																											

Answer Script Format:

Student ID:

Name:

Answer to the Question 1

Answer to the Question 2